

Lab

Submitted By: 2019PSP3023 Gargi Trivedi

Write a Tcd script to design a two-stage Op-Amp. Assume channel length = 1 μ m.

Op-Amp Specifications are:

$A_v = 5000$ V/V, $V_{DD} = 2.5$ V, $V_{SS} = -2.5$ V, $GB = 5$ Mhz, Phase Margin = 60 degree, $C_L = 10$ pF, $SR > 10$ V/ μ S, V_{out} range = plus minus 2V, $ICMR = -1$ to 2V, $P_{dissipation} < 2$ mW

Note: Design means to find the design parameter (aspect ratio) of all transistors to meet the specifications.

- ① $C_c > 0.22 C_L$
- ② $I_5 = SR \cdot C_c$
- ③ $S_3 = \frac{I_5}{K_3' [V_{DD} - V_{in(max)} - |V_{T02}|(max) + V_{T1}(min)]^2}$
- ④ $C_{gs3} \& C_{gs4} = 0.67 W_3 L_3 Cox$
 $\frac{g_{m3}}{2 C_{gs3}} > 10 GB$
Verify that pole ω_{p3} due to C_{gs3} and C_{gs4} will not be dominant by assuming it greater than $10 GB$.
- ⑤ Design for S_1 (S_2) to achieve desired GB
 $g_{m1} = GB C_c \rightarrow S_2 = \frac{g_{m2}^2}{K_2' I_5}$
- ⑥ S_5 from min. i/p length
 First calculate $V_{DS5}(sat.)$, then S_5
 $V_{DS5}(sat.) = V_{in}(min) - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T1}(max) \geq 100mV$
 $\rightarrow S_5 = \frac{2 I_5}{K_5' [V_{DS5}(sat.)]^2}$
- ⑦ S_6 is calculated by letting $p_2 = 2.2 GB$
 Assuming $V_{SG4} = V_{SG6}$
 $g_{m6} = 2.2 g_{m2} (C_L / C_c) \rightarrow S_6 = S_4 \frac{g_{m6}}{g_{m4}}$
- ⑧ $I_6 = \frac{g_{m6}^2}{2 K_6' S_6}$
- ⑨ $S_7 = (I_6 / I_5) S_5$

```
Terminal
gargi_assignment.tclsh x  scrp.tclsh x
set gm1 [expr 5*2*3.14*$Cc]
#(W/L)1=(W/L)2 =gm1^2/2Kn'I1
set s1 [expr ($gm1*$gm1)/(2*110*15)]
#To Calculate VDS5
set VDS5 .35
#To Calculate S5
set s5 [expr (2*$I5)/(11*$VDS5*$VDS5)/10]
#To calculate gm6
set gm6 [expr 10*$gm1]
#To calculate (W/L)6
#s6=(gm6/gm4)*s4
set s6 [expr (15*.0009425)/.00015]
#I6 using small signal gm expression
set I6 [expr pow(10, 11)*(.0009425*.0009425)/(2*5*$s6)]
#Finally calculating (W/L)7
set s7 [expr ($I6*$s5)/$I5]
puts "Calculated parameters for design are : "
puts "Coupling Capacitor $Cc pf"
puts "Tailing current $I5 micro Amperes"
puts "(W/L)3 is $s3"
puts "(W/L)1 is $s1"
puts "(W/L)2 is $s1"
puts "(W/L)5 is $s5"
puts "gm1 is $gm1 micro S"
puts "gm6 is $gm6 micro S"
puts "(W/L)6 is $s6"
puts "Current I6 using small signal expression is $I6 micro Amperes"
puts "Finally (W/L)7 is $s7"

gargi@gargi-Inspiron-5558: ~
gargi@gargi-Inspiron-5558:~$ tclsh scrp.tclsh
Calculated parameters for design are :
Coupling Capacitor 3.2 pf
Tailing current 35.2 micro Amperes
(W/L)3 is 3.348394768133175
(W/L)1 is 3.0594637575757586
(W/L)2 is 3.0594637575757586
(W/L)5 is 5.224489795918369
gm1 is 100.48000000000002 micro S
gm6 is 1004.8000000000002 micro S
(W/L)6 is 94.25
Current I6 using small signal expression is 94.25 micro Amperes
Finally (W/L)7 is 13.988868274582563
gargi@gargi-Inspiron-5558:~$
```

Code:

```
set Av 5000
set VDD 2.5
set VSS -2.5
set GB 5
set PhaseMargin 60
set CL 10
set SR 11
set Vout 2
set Pdissipation 1.9
set channel_lenght 1

# Cc > 2 CL
set Cc [expr (2.2*$CL)/10 +1]

# I5=SR*Cc
set I5 [expr $SR*$Cc]

# (W/L)3 using ICMR requirements
set s3 [expr $I5/(5*($VDD-2-2.5+.55)*($VDD-2-2.5+.55))]

#to calculate gm1
```

```
set gm1 [expr 5*2*3.14*$Cc]
```

```
 #(W/L)1=(W/L)2 =gm1^2/2Kn'I1
```

```
set s1 [expr ($gm1*$gm1)/(2*110*15)]
```

```
#To Calculate VDS5
```

```
set VDS5 .35
```

```
#To Calculate S5
```

```
set s5 [expr (2*$I5)/(11*$VDS5*$VDS5)/10]
```

```
#To calculate gm6
```

```
set gm6 [expr 10*$gm1]
```

```
#To calculate (W/L)6
```

```
#s6=(gm6/gm4)*s4
```

```
set s6 [expr (15*.0009425)/.00015]
```

```
#I6 using small signal gm expression
```

```
set I6 [expr pow(10, 11)*(.0009425*.0009425)/(2*5*$s6)]
```

```
#Finally calculating (W/L)7
```

```
set s7 [expr ($I6*$s5)/$I5]
```

```
puts "Calculated parameters for design are : "
```

```
puts "Coupling Capacitor $Cc pf"
```

```
puts "Tailing current $I5 micro Amperes"
```

```
puts "(W/L)3 is $s3"
```

```
puts "(W/L)1 is $s1"
```

```
puts "(W/L)2 is $s1"
```

```
puts "(W/L)5 is $s5"
```

```
puts "gm1 is $gm1 micro S"
```

```
puts "gm6 is $gm6 micro S"
```

```
puts "(W/L)6 is $s6"
```

```
puts "Current I6 using small signal expression is $I6 micro Amperes"
```

```
puts "Finally (W/L)7 is $s7"
```